

## Lab3 report

- Introduction about the overall system


- What is FIR

The term FIR abbreviation is “Finite Impulse Response” and it is one of two main types of digital filters used in DSP applications. This is its formula:


$$y[t] = \sum (h[i] * x[i-t])$$

- Overall design

- Block diagram

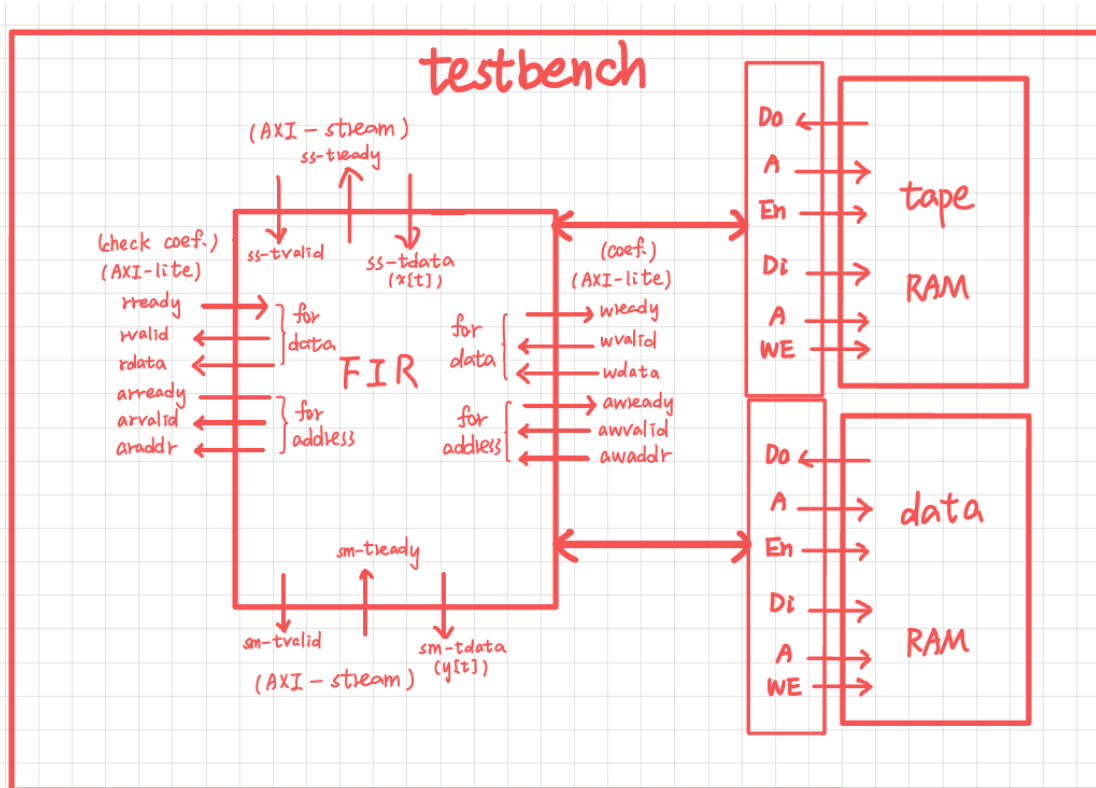


Overall view

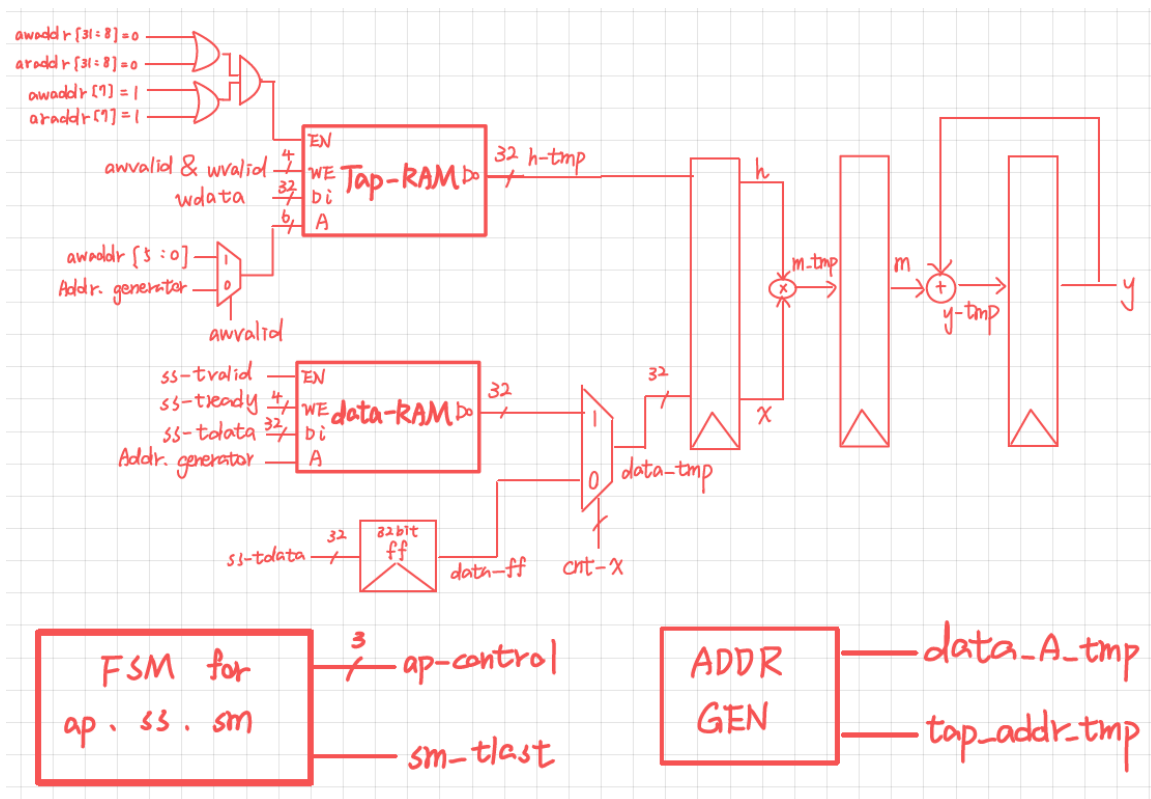


Block design in FIR

- Finite state machine

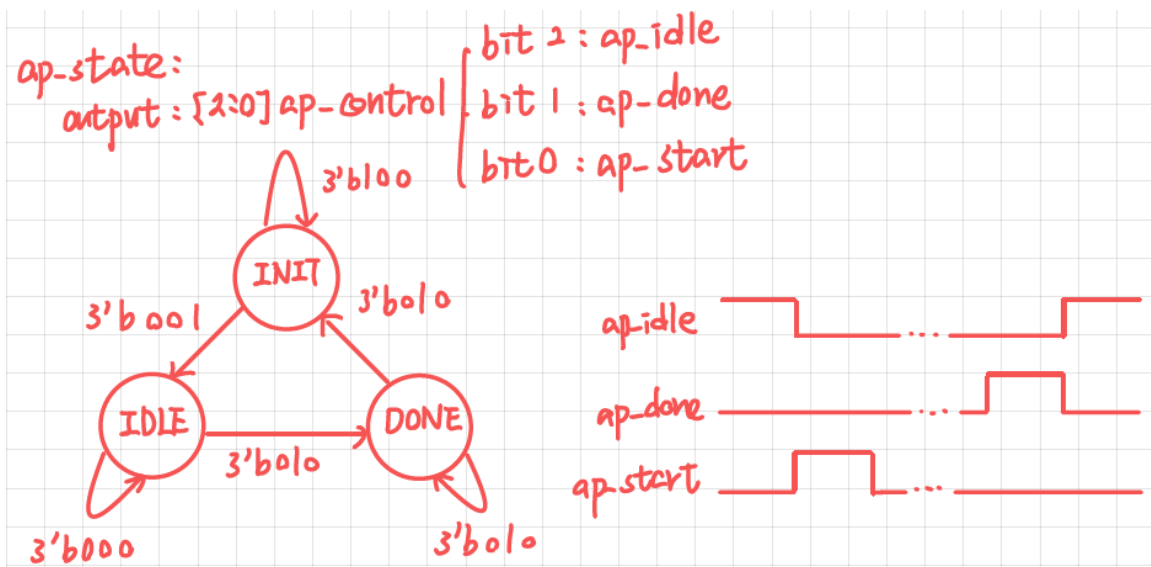

ap\_control

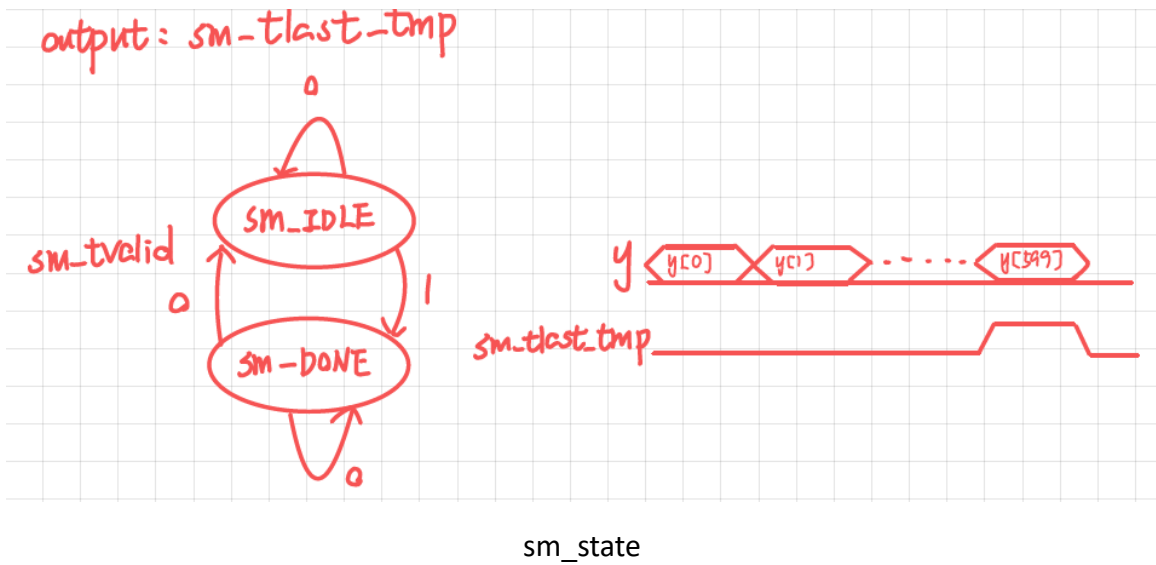

- Address generator

formula:  $y[t] = \sum_{i=0}^{10} h[i] \times x[t-i]$

o If we save  $h[i]$  like this

$h[0]$	$h[1]$	$h[2]$	...	...	$h[10]$
80	84	88	...	...	ac

(address)

then for each  $y[t]$  operation, we need to read data from 0 to 10, so address generator of tap ram is like this:

$12'h080 + 4 * k, k \text{ from } 0 \sim 10$

Address generator for tap RAM

② if we save  $x[t]$  like this



then we need to do two things:

1. shift left when calculate each  $y[t]$
2. every  $y[t]$  has different starting point, it is  $x[t-0] = x[t]$
3. replace oldest  $x[t]$  by new one, since we had 600  $x$  data but 11 to save.

so address generator of data RAM is like this:

$$4 * (l - k) \quad , \text{ if } l - k > 0$$
$$4 * (11 + l - k) \quad , \text{ if } l - k < 0$$


$k$  count every cycle, (for shift left)

$l$  count every eleven cycle (for new starting point)
 
#### Address generator for data RAM


- How do data and tap RAM read and write data?

If EN is 1 and WE is 1, then we can write the data to RAM (stage 3 and 7 in waveform below). If EN is 1 and WE is 0, then we can read the data in RAM (stage 2, 4 and 6 in waveform below). If EN is 0, we can't read and write the data in RAM.



Waveform

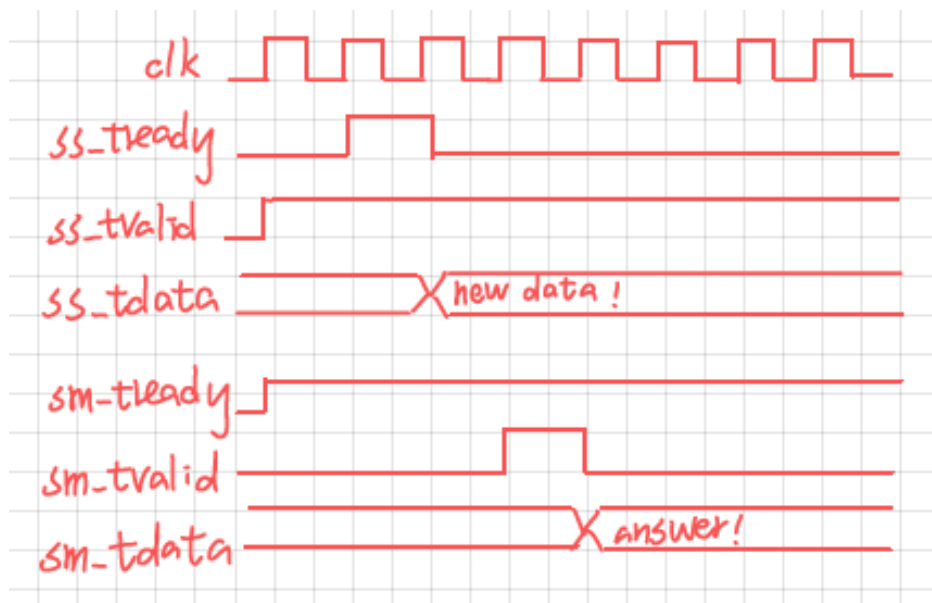
- How to input data and receive the answer?  
To receive the data in testbench, we set the `ss_tvalid` to 1, so when `ss_tready` is trigger, data will pass to our design in next cycle. To pass back the answer to testbench to check answer correct or not, we set `sm_tready` to 1, so when `ss_tvalid` is trigger, data will pass to testbench in next cycle.



AXI\_stream design

- How does the pipeline operation processing?

 Look in the design of RAM, we can receive data in next cycle after the address input. And we use a flipflop to save data output, multiplication result( $m[i] = h[i] * x[t-i]$ ), sigma result ( $y[t] = \sum m[i]$ ), and then finally output answer.



Pipeline operation

- Screen dump
  - Resources usage

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	175	0	0	53200	0.33
LUT as Logic	175	0	0	53200	0.33
LUT as Memory	0	0	0	17400	0.00
Slice Registers	201	0	0	106400	0.19
Register as Flip Flop	201	0	0	106400	0.19
Register as Latch	0	0	0	106400	0.00
F7 Muxes	0	0	0	26600	0.00
F8 Muxes	0	0	0	13300	0.00

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	140	0.00
RAMB36/FIFO*	0	0	0	140	0.00
RAMB18	0	0	0	280	0.00

- Timing report

# Design Timing Summary


WNS(ns)	TNS(ns)	TNS Failing Endpoints	TNS Total Endpoints	WHS(ns)	THS(ns)
0.168	0.000	0	473	0.142	0.000

## Timing summary


Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
	(clock FIR_clk rise edge)	0.000	0.000	r
	net (fo=0)	0.000	0.000	r axis_clk (IN)
	IBUF (Prop_ibuf_I_0)	0.972	0.972	r axis_clk_IBUF_inst/0
	net (fo=1, unplaced)	0.800	1.771	r axis_clk_IBUF
	BUF (Prop_bufg_I_0)	0.101	1.872	r axis_clk_IBUF_BUF inst/0
	net (fo=201, unplaced)	0.584	2.456	r axis_clk_IBUF_BUF
	FDPE			r cnt_y_reg[0]/C
	FDPE (Prop_fdpe_C_Q)	0.478	2.934	f cnt_y_reg[0]/Q
	net (fo=8, unplaced)	0.844	3.778	cnt_y[0]
	LUT5 (Prop_lut5_I0_0)	0.295	4.073	r sm_tvalid_OBUF_inst_i_1/0
	net (fo=74, unplaced)	0.541	4.614	sm_tvalid_OBUF
	LUT6 (Prop_lut6_I2_0)	0.124	4.738	r tlast_cnt[9]_i_2/0
	net (fo=5, unplaced)	0.477	5.215	tlast_cnt[9]_i_2_n_0
	LUT6 (Prop_lut6_I3_0)	0.124	5.339	r rdata_OBUF[1]_inst_i_8/0
	net (fo=1, unplaced)	0.449	5.788	rdata_OBUF[1]_inst_i_8_n_0
	LUT6 (Prop_lut6_I5_0)	0.124	5.912	r rdata_OBUF[1]_inst_i_4/0
	net (fo=1, unplaced)	0.000	5.912	rdata_OBUF[1]_inst_i_4_n_0
	CARRY4 (Prop_carry4_S[2]_CO[3])	0.380	6.292	r rdata_OBUF[1]_inst_i_2/CO[3]
	net (fo=5, unplaced)	0.946	7.238	rdata_OBUF[1]_inst_i_2_n_0
	LUT6 (Prop_lut6_I0_0)	0.124	7.362	rdata_OBUF[1]_inst_i_1/0
	net (fo=1, unplaced)	0.800	8.162	rdata_OBUF[1]
	OBUF (Prop_obuf_I_0)	2.634	10.797	r rdata_OBUF[1]_inst/0
	net (fo=0)	0.000	10.797	rdata[1]
				r rdata[1] (OUT)
	(clock FIR_clk rise edge)	10.000	10.000	r
	clock pessimism	0.000	10.000	
	clock uncertainty	-0.035	9.965	
	output delay	1.000	10.965	
	required time		10.965	
	arrival time		-10.797	
	slack		0.168	

## Slack


### Simulation waveform

 


## Coefficient read back

 

 Data in stream in and data out stream out



RAM access control

 

FSM

Clock cycles from ap\_start to ap\_done:

$$\frac{done\ timing - start\ timing}{clock\ period} = \frac{66625ns - 595ns}{10ns} = 6603cycls$$

- 遲交原因：自己的時間管理不當，加上清大停電導致工作站無法使用，影響其他科目像是類比設計與分析與積體電路設計導論的進度，進而影響 SOC 的進度。還有即將完成時，電腦當機送修一個禮拜，由於檔案上外上傳，於是借了朋友的電腦重做了一次，導致無法預期完成，相當抱歉。